## Jenny Vaccaro

CompArch HW2 Writup:

## # Behavioral Decoder

# En A0 A1 | | O0 O1 O2 O3 | Expected Output

#000| 000 All false

#0 1 0 || 0 0 0 0 | All false

#0 0 1 || 0 0 0 0 | All false

#0 1 1 || 0 0 0 0 | All false

#100||1000|O0Only

#110||0100|O1Only

#1 0 1 || 0 0 1 0 | O2 Only

#111||0001|03 Only

## # Structural Decoder

# En A0 A1 | | O0 O1 O2 O3 | Expected Output

#000||000|All false

# 0 1 0 || 0 0 0 0 | All false

#001||000|All false


# 0 1 1 || 0 0 0 0 | All false

#1 0 0 || 1 0 0 0 | 00 Only

#1 1 0 || 0 1 0 0 | O1 Only

#101||0010|O2Only

#111||0001|O3Only

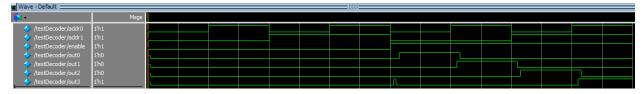

## # Behavioral Multiplexer

# A0 A1 | in0 in1 in2 in3 | Out | Expected Output

#00|000||0|False

#0 0| 1 0 0 0 || 1 | True

#0 0| 1 1 1 1 || 1 | True

#1 0 | 0 0 0 0 | 0 | False

#10|0100||1|True

#10|111||1|True

#0 1 0 0 0 0 0 | 0 False

#0 1 0 0 1 0 | 1 | True

#0 1 | 1 1 1 1 | 1 | True

#1 1 0 0 0 0 | 0 | False

#1 1 0 0 0 1 | 1 | True

#1 1 | 1 1 1 1 | 1 | True

```
# Structural Multiplexer
# A0 A1 | in0 in1 in2 in3 | Out | Expected Output
#0 0| 0 0 0 0 || 0 | False
#0 0| 1 0 0 0 || 1 | True
#0 0| 1 1 1 1 || 1 | True
#1 0 0 0 0 0 | 0 | False
#1 0| 0 1 0 0 || 1 | True
#1 0 | 1 1 1 1 | 1 | True
#0 1 0 0 0 0 | 0 False
#0 1 0 0 1 0 1 1 True
#0 1 | 1 1 1 1 | 1 | True
#1 1 0 0 0 0 | 0 | False
#1 1 0 0 0 1 | 1 | True
#1 1 | 1 1 1 1 | 1 | True
# Behavioral FullAdder
# A B CarryIn | | Sum CarryOut | Expected Output
#000| O | All false
#0 0 1 || 1 0 | Sum only
#0 1 0 || 1 0 | Sum only
#0 1 1 | 0 1 | Carryout only
#1 0 0 || 1 0 | Sum only
#1 0 1 | 0 1 | CarryOut only
#1 1 0 || 0 1 | CarryOut only
#111||11|All true
# Structural FullAdder
# A B CarryIn || Sum CarryOut | Expected Output
#000| O | All false
#0 0 1 || 1 0 | Sum only
#0 1 0 || 1 0 | Sum only
#0 1 1 || 0 1 | Carryout only
#1 0 0 || 1 0 | Sum only
#1 0 1 | 0 1 | CarryOut only
#1 1 0 || 0 1 | CarryOut only
#111||11|All true
```